
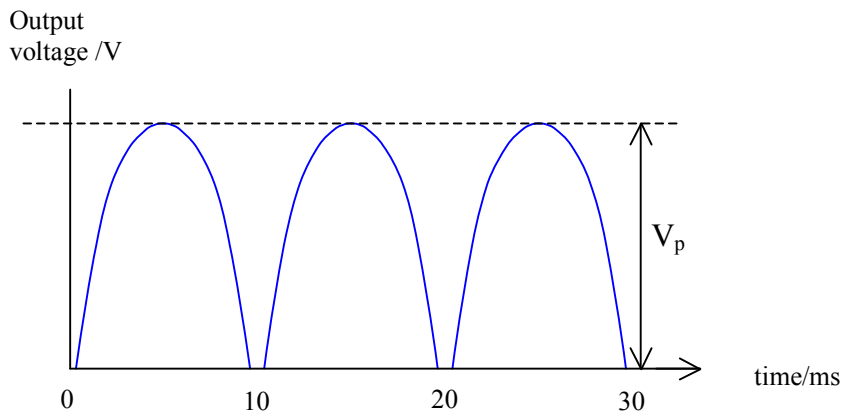


Calculating Ripple Voltage (V_{ripple})

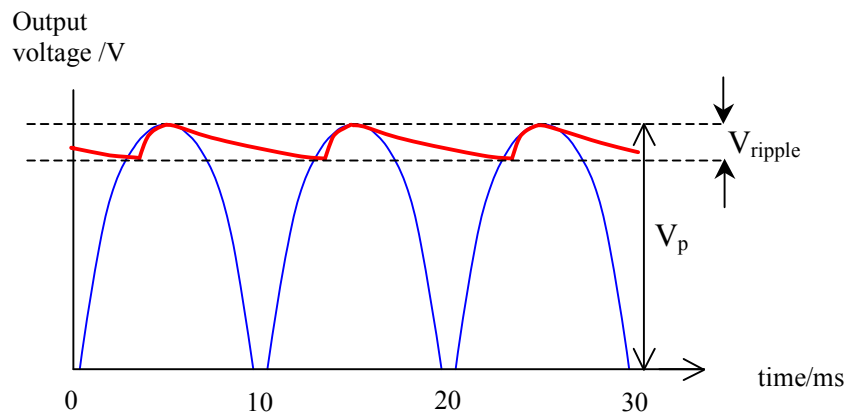The **output** from a full-wave bridge rectifier looks like this:



If we add a smoothing capacitor the capacitor charges up to the peak value of voltage and the output stays steady at this value ... until you connect a load to the power supply (R_L). Now the **output** will look like this:



As the output voltage from the bridge drops the capacitor discharges through the load and so a **ripple voltage**, V_{ripple} , appears on the output from the supply.

The size of this voltage depends on the load resistance, R_L , the size of the smoothing capacitor, C , and the peak value of the output voltage, V_p , and is given by:

$$V_{\text{ripple}} = \frac{V_p}{R_L C} \times \Delta t$$

where Δt is the time between successive peaks of the output waveform from the rectifier circuit. This will be 10ms if the ac frequency is 50Hz and a full-wave bridge rectifier circuit is used. (But **20ms** if a half-wave rectifier circuit is used; the question could specify a ***different supply frequency***, eg 60Hz, which would also affect Δt .)

This formula is an approximation and assumes that the ripple voltage is small. If the ripple voltage exceeds ~10% this formula becomes increasingly inaccurate.